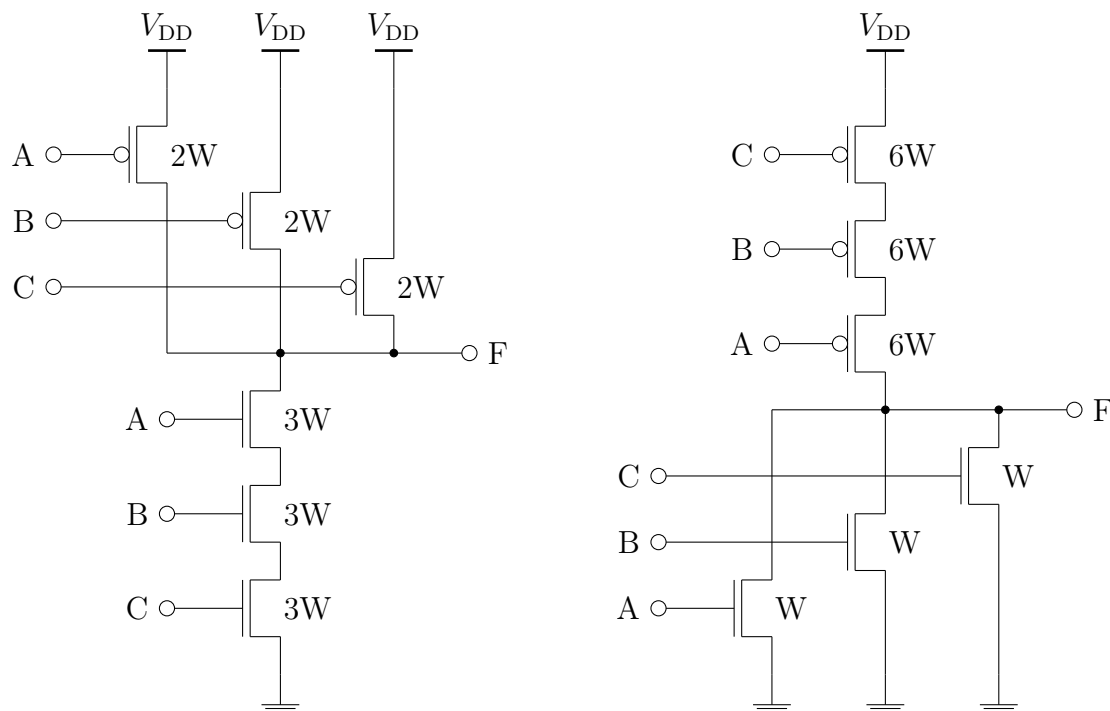


### Solution 7.1


We get the sizing in Fig. 7.5. Both implementations have about the same delay for rising and falling edges as the CMOS inverter.



**Figure 7.5:** NAND3-Gate (a), NOR3-Gate (b)

### Solution 7.2

Fig. 7.6 shows the realization of the AND8 function as a two-stage digital circuit. Fig. 7.7 shows the realization of the function AND8 as a three-level digital circuit.

 

**Figure 7.6:** NAND4-NOR2

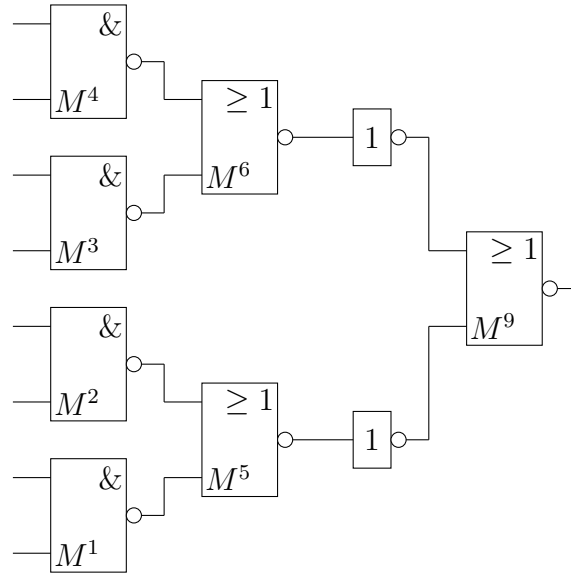


Figure 7.7: NAND2-NOR2-INV-NOR2

## Solution 7.3

- a) If one input (i) is at  $V_{DD}$  and the other input goes from 0 to  $V_{DD}$ , this is equivalent to a pull-up of  $W_P = 400\text{nm}$  and a pull-down of  $W_N = 400\text{nm}$ :

$$W_N = 0.4\mu\text{m} \quad W_P = 0.4\mu\text{m}$$

$$\chi = \sqrt{\frac{\frac{W_N}{E_{CN}L_N}}{\frac{W_P}{E_{CP}L_P}}} = \sqrt{\frac{W_N E_{CP}}{W_P E_{CN}}} = \sqrt{\frac{0.4 \cdot 10^{-6}\text{m}(24 \cdot 10^4\text{V/cm})}{0.4 \cdot 10^{-6}\text{m}(6 \cdot 10^4\text{V/cm})}} = 2.0$$

$$V_S = \frac{V_{DD} - |V_{TP}| + \chi V_{TN}}{1 + \chi} = \frac{1.8\text{V} - |-0.5\text{V}| + 2.0(0.5\text{V})}{1 + 2.0} = 0.77\text{V}$$

If both inputs (ii) go simultaneously from 0 to  $V_{DD}$ , this is equivalent to a pull-up of  $W_P = 800\text{nm}$  and a pull-down of  $W_N = 200\text{nm}$ :

$$W_N = 0.2\mu\text{m} \quad W_P = 0.8\mu\text{m}$$


$$\chi = \sqrt{\frac{\frac{W_N}{E_{CN}L_N}}{\frac{W_P}{E_{CP}L_P}}} = \sqrt{\frac{W_N E_{CP}}{W_P E_{CN}}} = \sqrt{\frac{0.2 \cdot 10^{-6}\text{m}(24 \cdot 10^4\text{V/cm})}{0.8 \cdot 10^{-6}\text{m}(6 \cdot 10^4\text{V/cm})}} = 1.0$$

$$V_S = \frac{V_{DD} - |V_{TP}| + \chi V_{TN}}{1 + \chi} = \frac{1.8\text{V} - |-0.5\text{V}| + 1.0(0.5\text{V})}{1 + 1.0} = 0.9\text{V}$$


- b) Solution in SPICE:

As expected, the curve with the two connected inputs is on the right side of the transfer characteristic of an inverter. For the transition at A,  $V_S = 0.745\text{V}$ , for the transition at B,  $V_S = 0.721\text{V}$ , for A and B is common  $V_S \approx 0.9\text{V}$ . These values are close to a manual calculation. Hand calculations tend to have slightly higher values due to the approximations for  $V_S$ . The reason input A returns a slightly

higher value of  $V_S$  is because the corresponding transistor has a body effect ( $V_{SB}$ ) during switching.

 

**Figure 7.8:** Solution in SPICE

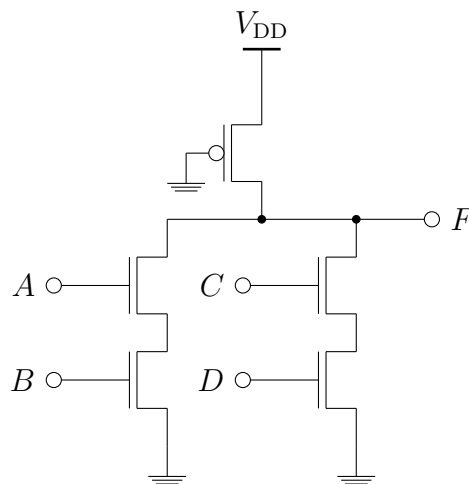

**Figure 7.9:** Implementation of a Pseudo-NMOS Inverter

---

#### Solution 7.4

---


The n-complex is obtained by coding the zeros as ones.

$$\overline{PD}(A, B, C, D) = AB + CD$$

Thus, two paths with transistors are arranged in series parallel to each other in the n-complex. One path implements  $AB$ , the other  $CD$ . The dual and component complementary statement of  $\overline{PD}$  results in the circuit of the p-complex.

$$PU(A, B, C, D) = (\overline{A} \vee \overline{B})(\overline{C} \vee \overline{D})$$

For the pseudo-NMOS, only the n-complex is needed. The pull-up network consists of a single PMOS transistor. The pseudo-NMOS is therefore more efficient in terms of area than the CMOS (see Fig. 7.9).

 

**Figure 7.10:** Single stage CMOS Complex

### Solution 7.5

It applies  $V_{OL} = 0V$  and  $V_{OH} = V_{DD}$


$A$	$B$	$C$	$D$	$F$
0	0	1	$Z$	1
0	1	0	0	0
1	0	1	$Z$	0
1	1	0	0	0

### Solution 7.6

In the following, the cross-coupled NOR configuration in Fig. 7.11 is used. To get the desired runtimes we use the relation  $t_{PHL} = t_{PLH} = 0.7R_{eff}C_L$ . There is double the runtime from  $S$  to  $Q$  and from  $R$  to  $\bar{Q}$ . Therefore, we evenly divide the two delays between the two NOR gates. For the n complex,  $R_{eqn} = 12.5k\Omega$  applies.

$$t_{PHL} = 0.7(12.5k\Omega)\frac{L}{W}(100fF) = 200ps \quad \Leftrightarrow \quad \frac{W}{L} = 4.4$$

Set  $W_N = 440nm$  for both NMOS gates. For the PMOS gates we then use four times the size of the NMOS gates,  $W_P = 1.76\mu m$ .

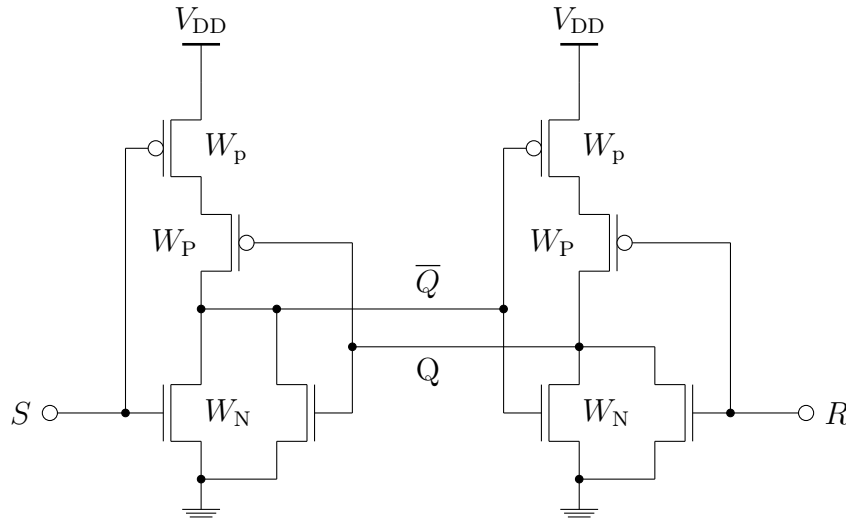

**Figure 7.11:** Schematic of a RS-Latch

### Solution 7.7

Due to the biasing of the NMOS load by the pull-down no VDD-one can be reached.

$$V_{OH} = V_{DD} - V_{TL}(V_{SB}) = V_{DD} - \left( V_{T0} + \gamma \left( \sqrt{V_{SB} + 2|\phi_F|} - \sqrt{2|\phi_F|} \right) \right)$$

Together with  $V_{SB} = V_{OH} \neq 0$  bzw.  $X = \sqrt{V_{OH} + 2|\phi_F|}$  follows

$$X^2 + 2X\frac{\gamma}{2} + \left(\frac{\gamma}{2}\right)^2 = V_{DD} - V_{T0} + 2|\phi_F| + \gamma\sqrt{2|\phi_F|} + \left(\frac{\gamma}{2}\right)^2$$

with

$$\begin{aligned} V_{DD} - V_{T0} + 2|\phi_F| + \gamma\sqrt{2|\phi_F|} + \left(\frac{\gamma}{2}\right)^2 &= A \\ \left(X + \frac{\gamma}{2}\right)^2 &= A \\ X &= \sqrt{A} - \frac{\gamma}{2} \end{aligned} \tag{7.1}$$

and

$$\begin{aligned} V_{OH} &= \left(\sqrt{A} - \frac{\gamma}{2}\right)^2 - 2|\phi_F| \\ V_{OH} &= A - \gamma\sqrt{A} + \frac{\gamma^2}{4} - 2|\phi_F| \\ V_{OH} &= (V_{DD} - V_{T0}) + \left(\frac{\gamma}{2} + \sqrt{2|\phi_F|}\right)^2 - \gamma\sqrt{A} + \frac{\gamma^2}{4} - 2|\phi_F| \\ V_{OH} &= (V_{DD} - V_{T0}) + \frac{\gamma}{2} \left( \gamma + 2\sqrt{2|\phi_F|} - 2\sqrt{A} \right) \end{aligned} \tag{7.2}$$

with  $B = \gamma + 2 \left( \sqrt{2|\phi_F|} - \sqrt{A} \right)$  follows

$$A = 1.2V - 0.4V + 0.88V + 0.2V^{1/2}\sqrt{0.88V} + \left(\frac{0.2V}{2}\right)^2 = 1.8776V$$

$$B = 0.2V^{1/2} + 2 \left( \sqrt{0.88V} - \sqrt{1.8776V} \right) = -0.664V^{1/2}$$

$$V_{OH} = 1.2V - 0.4V + \frac{0.2V^{1/2}}{2} \cdot (-0.664V^{1/2}) = 0.7336V$$

$$V_{TL}(V_{OH}) = 0.4V + 0.2V^{1/2} \left( \sqrt{1.8776V} - \frac{0.2V^{1/2}}{2} - \sqrt{0.88V} \right) = 0.4664V$$

(2nd variant to find  $V_{OH}$  see solution 6.1)

$$K_R \frac{\mu_n}{L} \left( (V_{DD} - V_{TI}) - \frac{V_{OL}}{2} \right) V_{OL} \left( \frac{1}{1 + \frac{V_{OL}}{E_{CN}L}} \right) = \frac{\nu_{sat} (V_{DD} - V_{OL} - V_{TL})^2}{(V_{DD} - V_{OL} - V_{TL}) + E_{CN}L} \quad (7.3)$$

$$V_{TL} = V_{T0} + \gamma \left( \sqrt{V_{OL} + 2|\phi_F|} - \sqrt{2|\phi_F|} \right) \quad (7.4)$$

Insert  $V_{OL}$  in Equ. (7.3) (iterative) and calculate  $K_R$  (for  $K_R=1$  finished)

$$\Rightarrow V_{OL} = 0.165V$$

$$I_{DC} = W v_{sat} C_{ox} \frac{(V_{DD} - V_{TL} - V_{OL})^2}{(V_{DD} - V_{TL} - V_{OL}) + E_{CN}L_N}$$

$$I_{DC} = (0.1 \cdot 10^{-4} \text{cm})(8 \cdot 10^6 \text{cm s}^{-1})(1.6 \cdot 10^{-6} \text{F cm}^{-2}) \frac{(1.2V - 0.46V - 0.165V)^2}{(1.2V - 0.46V - 0.165V) + 0.6V} = 36\mu A$$

$$P_{DC} = I_{DC} V_{DD} = 36\mu A \cdot 1.2V = 43.2\mu W$$