

Solution 11.1

$$\text{a) } LE(A) = \frac{(C_{\text{in}}R_{\text{on}})_{\text{gate}}}{(C_{\text{in}}R_{\text{on}})_{\text{inv}}} = \frac{4W(2R)}{3W(R)} = \frac{8}{3}$$

$$LE(S) = \frac{(C_{\text{in}}R_{\text{on}})_{\text{gate}}}{(C_{\text{in}}R_{\text{on}})_{\text{inv}}} = \frac{W(2R)}{3W(R)} = \frac{2}{3}$$

$$\text{b) } LE(A) = \frac{(C_{\text{in}}R_{\text{on}})_{\text{gate}}}{(C_{\text{in}}R_{\text{on}})_{\text{inv}}} = \frac{4W(5R/4)}{3W(R)} = \frac{5}{3}$$

$$LE(S) = \frac{(C_{\text{in}}R_{\text{on}})_{\text{gate}}}{(C_{\text{in}}R_{\text{on}})_{\text{inv}}} = \frac{4W(5R/4)}{3W(R)} = \frac{5}{3}$$

Solution 11.2

a) For equal rise and fall times we double the size of the transistors:

$$LE(A) = \frac{(C_{\text{in}}R_{\text{on}})_{\text{gate}}}{(C_{\text{in}}R_{\text{on}})_{\text{inv}}} = \frac{C_{\text{g}} \cdot 3W \cdot R_{\text{eqn}}}{C_{\text{g}} \cdot 3W \cdot R_{\text{eqn}}} = 1$$

b) For the pseudo-NMOS we first have to calculate the ratio of the currents, since these are different for the PMOS and NMOS. In case of the pull-up the PMOS charges the output, so for the same delay the output is doubled:

$$LE(B) = \frac{(C_{\text{in}}R_{\text{on}})_{\text{gate}}}{(C_{\text{in}}R_{\text{on}})_{\text{inv}}} = \frac{C_{\text{g}} \cdot 2W \cdot R_{\text{eqn}}}{C_{\text{g}} \cdot 3W \cdot R_{\text{eqn}}} = \frac{2}{3}$$

Solution 11.3

The results for a two-stage multiplexer ($R_{\text{inv}} = R$, $R_{\text{TG}} = R$) are

$$\begin{aligned} C_1 &= C_{\text{in,TG,on}} + C_{\text{self,inv}} \\ &= (C_{\text{eff}}2W + C_{\text{g}}W) + C_{\text{eff}}3W \\ &= C_{\text{eff}}5W + C_{\text{g}}W \end{aligned}$$

$$\begin{aligned} C_2 &= C_{\text{out,TG,on}} + C_{\text{out,TG,off}} + C_{\text{in,TG,on}} \\ &= (C_{\text{eff}}2W + C_{\text{g}}W) + C_{\text{eff}}2W + (C_{\text{eff}}2W + C_{\text{g}}W) \\ &= C_{\text{eff}}6W + C_{\text{g}}2W \end{aligned}$$

$$\begin{aligned} C_3 &= C_{\text{out,TG,on}} + C_{\text{out,TG,off}} + C_{\text{in,inv}} \\ &= (C_{\text{eff}}2W + C_{\text{g}}W) + C_{\text{eff}}2W + C_{\text{g}}3W \\ &= C_{\text{eff}}4W + C_{\text{g}}(1 + 3f)W \end{aligned}$$

$$t_{\text{Elmore,2MUX}} = R_1C_1 + (R_1 + R_2)C_2 + (R_1 + R_2 + R_3)C_3$$

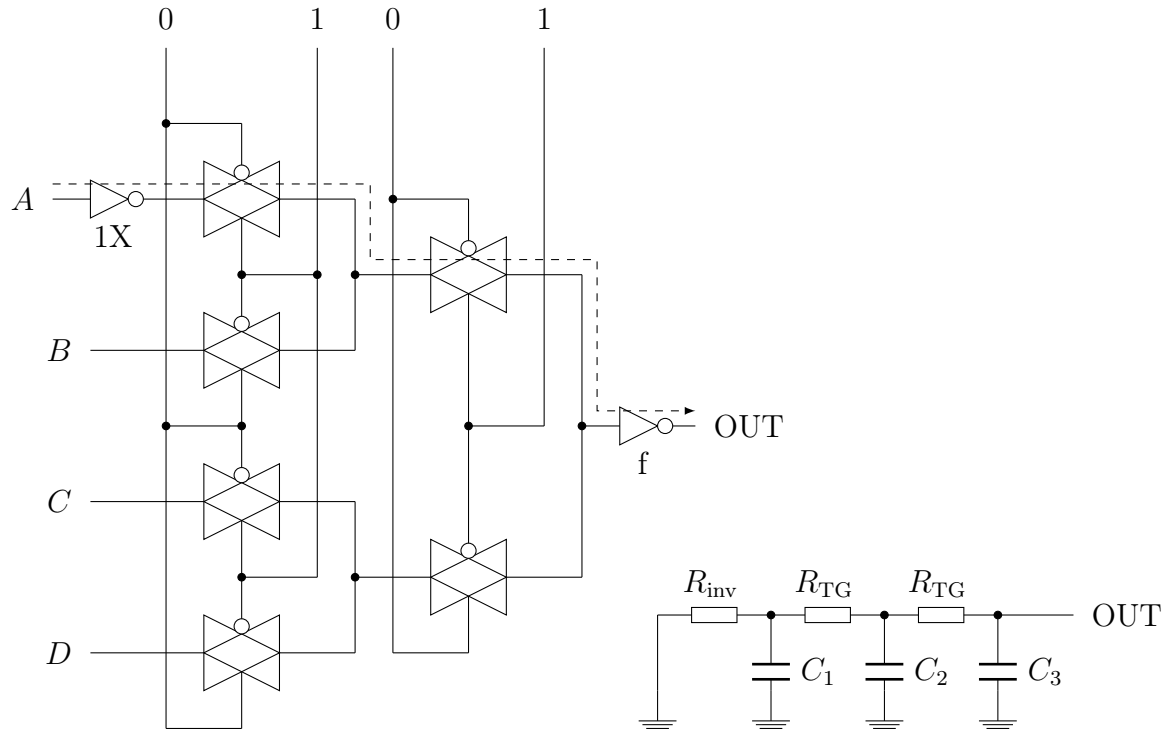


Figure 11.6: Two-Stage Multiplexer (2MUX)

$$\begin{aligned}
 &= R_{\text{inv}}C_1 + (R_{\text{inv}} + R_{\text{TG}})C_2 + (R_{\text{inv}} + 2R_{\text{TG}})C_3 \\
 &= R(29C_{\text{eff}} + 8C_g + 9fC_g)W
 \end{aligned}$$

and for a single-stage multiplexer ($R_{\text{inv}} = R$, $R_{\text{TG}} = R$)

$$\begin{aligned}
 C_4 &= C_{\text{in,TG,on}} + C_{\text{self,inv}} \\
 &= (C_{\text{eff}}2W + C_gW) + C_{\text{eff}}3W \\
 &= C_{\text{eff}}5W + C_gW \\
 C_5 &= C_{\text{TG,on}} + 3C_{\text{TG,off}} + C_{\text{in,inv}} \\
 &= C_{\text{eff}}2W + C_gW + 3C_{\text{eff}}2W + C_gf3W \\
 &= C_{\text{eff}}8W + C_g(1 + 3f)W
 \end{aligned}$$

$$\begin{aligned}
 t_{\text{Elmore,1MUX}} &= R_4C_4 + (R_4 + R_5)C_5 \\
 &= RC_{\text{eff}}21W + RC_g(3 + 6f)W \\
 &= R(21C_{\text{eff}} + 3C_g + 6fC_g)W
 \end{aligned}$$

Comparing the two cases, 2MUX is slower than 1MUX. However, 1MUX requires more routing resources.

Many transfer gates without buffering quickly increase the delay. For driving a large load, TGs do not have the necessary driver capability.


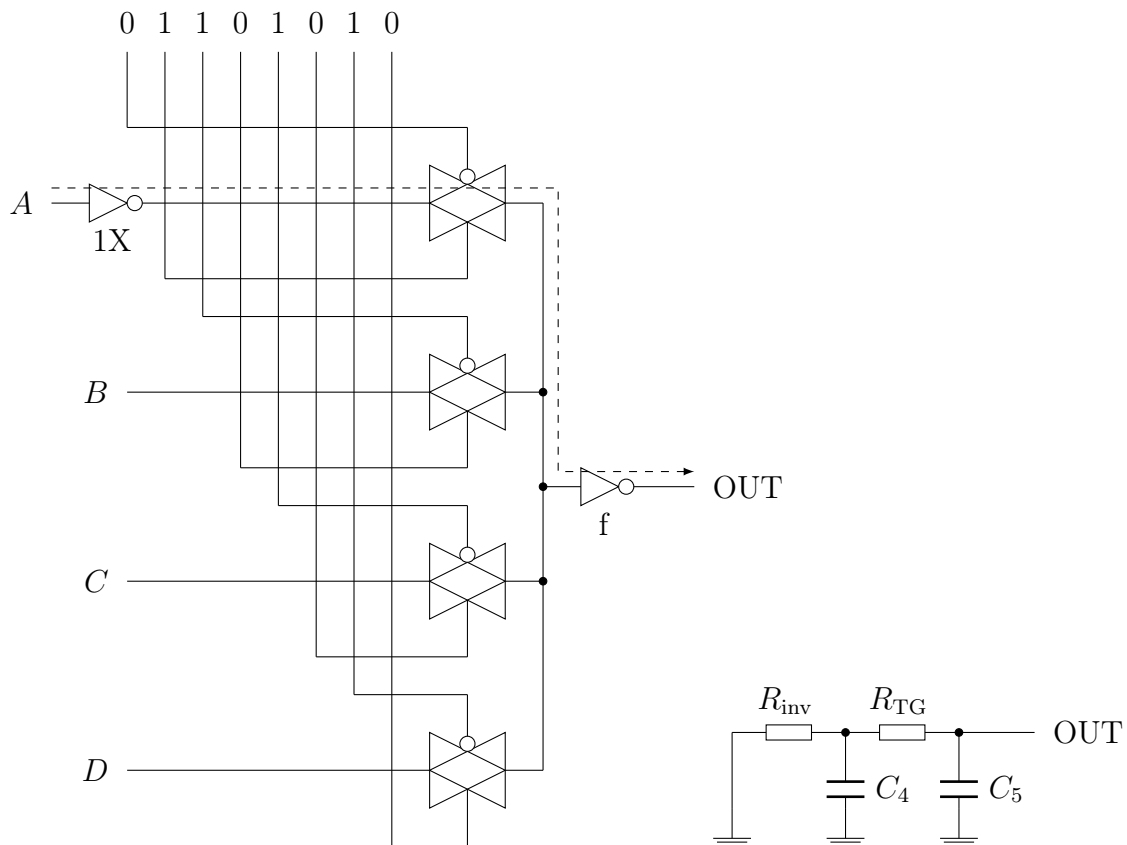




Figure 11.7: One-stage Multiplexer (1MUX)

Solution 11.4

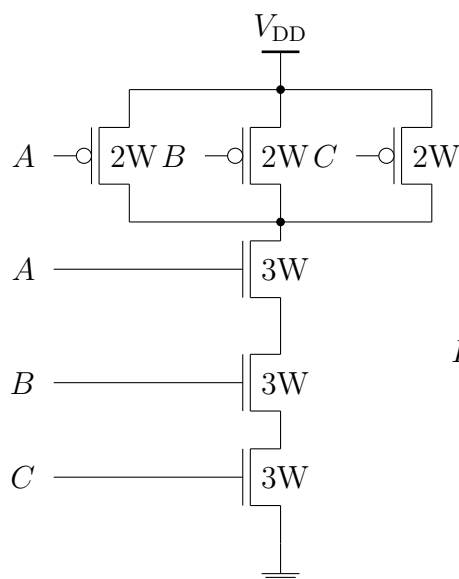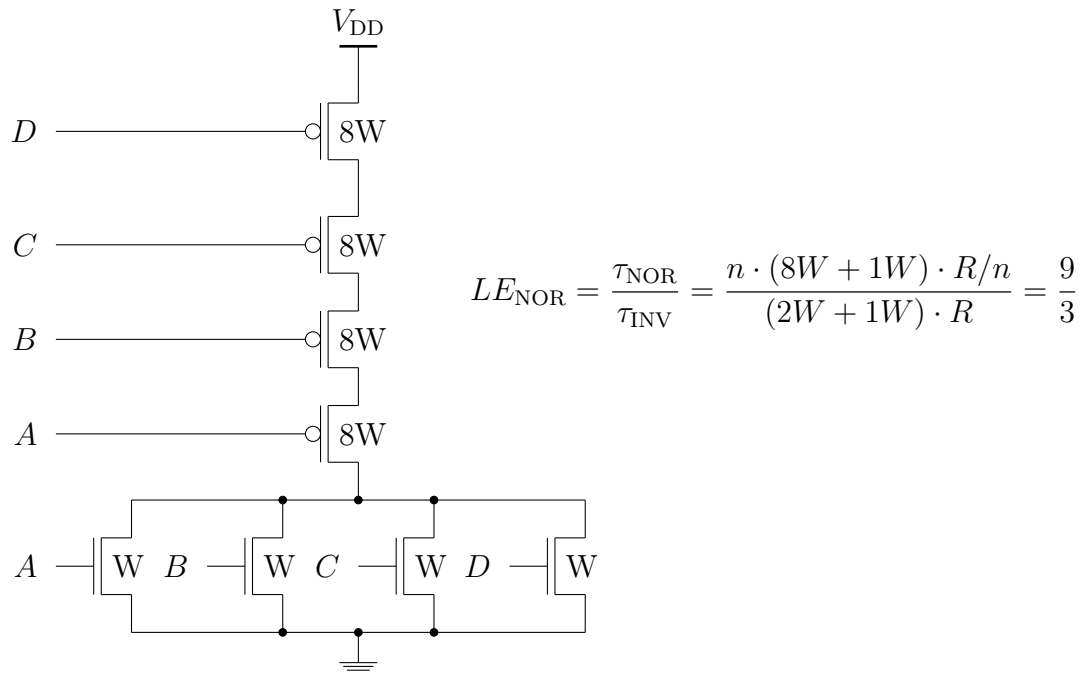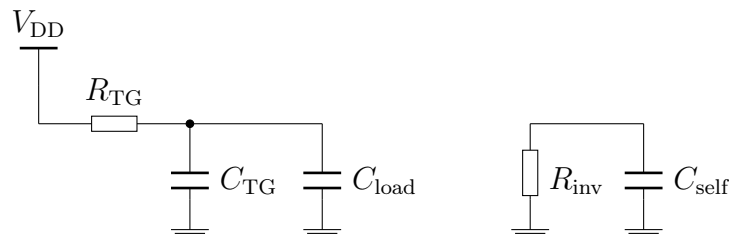

$$LE_{\text{NAND}} = \frac{\tau_{\text{NAND}}}{\tau_{\text{INV}}} = \frac{n \cdot (2W + 3W) \cdot R/n}{(2W + 1W) \cdot R} = \frac{5}{3}$$

Figure 11.8: NAND3

**Figure 11.9: NOR4****Solution 11.5****Figure 11.10: Equivalent Circuit Diagram**

$V_Q = V_{DD} = 1,8\text{V}$ and $V_{\bar{Q}} = 0\text{V}$. The clock feedthrough has no effect, because PMOS dominates. For a CLK of $0 \rightarrow 1$ the TG is in the ON state.

For the CLK (A is already switched) dependent delay of \bar{Q} follows

$$\begin{aligned}
 t_{\text{PHL}} &= R_{\text{TG}}(C_{\text{TG}} + C_{\text{load}}) + R_{\text{inv}}C_{\text{self}} \\
 &= R_{\text{eqn}}(C_g + 2C_{\text{eff}} + 3C_g + 3C_{\text{eff}})W \\
 &= (12,5 \cdot 10^3 \Omega)(2 + 2 \cdot 1 + 3 \cdot 2 + 3 \cdot 1)(10^{-15} \text{F})(0,2) \\
 &= 25\text{ps} + 7,5\text{ps} \\
 &= 32,5\text{ps}
 \end{aligned}$$