

**Figure 6.1:** NMOS Inverter

---

### Task 6.1

---

Fig. 6.1 shows a pull-up transistor. Specify whether the transistor is operating in the saturation or cut-off range during operation and calculate the output voltage high ( $V_{OH}$ ). Use the values of a  $0.13\mu\text{m}$  technology ( $2|\Phi_F| = 0.88\text{V}$ ,  $\gamma = 0.2\text{V}^{1/2}$ ).

---

### Task 6.2

---

Design an inverter with a NMOS load. For the input voltage  $V_{in} = V_{DD}$  an output level  $V_{OL} = 0.1\text{V}$  is required. Use the values of a  $0.13\mu\text{m}$  technology ( $\mu_n = 270\text{cm}^2/\text{Vs}$ ,  $E_{CN}L = 0.6\text{V}$ ,  $v_{sat} = 8 \cdot 10^6\text{cm/s}$ ).

---

### Task 6.3

---

Derive the general formulas  $V_{IL}$ ,  $V_{IH}$  and  $V_{OIH}$  for the CMOS inverter in Fig. 6.2. The NMOS transistor is in saturation range, the PMOS transistor in linear range.


---

### Task 6.4

---

Compare the voltage transfer characteristic from a SPICE calculation with the results of a manual calculation for a CMOS inverter (Fig. 6.2) with  $W_N = 400\text{nm}$  and  $W_P = 800\text{nm}$ . Use the values of a  $0.18\mu\text{m}$  CMOS technology ( $\mu_n = 270\text{cm}^2/\text{Vs}$ ,  $\mu_p = 70\text{cm}^2/\text{Vs}$ ,  $C_{ox} = 1\mu\text{F}/\text{cm}^2$ ,  $V_{TN} = 0.5\text{V}$ ,  $V_{TP} = -0.5\text{V}$ ,  $V_{DD} = 1.8\text{V}$ ,  $L = 200\text{nm}$ ,  $E_{CN}L = 1.2\text{V}$ ,  $E_{CP}L = 4.8\text{V}$ ,  $v_{sat} = 8 \cdot 10^6\text{cm/s}$ ).

---

 

**Figure 6.2:** CMOS Inverter

---

### Task 6.5

---

Calculate the switching point  $V_S$  of a CMOS inverter with  $W_P = 400\text{nm}$  and  $W_P = 100\text{nm}$ . In both cases  $W_N = 100\text{nm}$  applies. How do changes from  $W_P$  affect  $V_S$ ? Use the values of a  $0.13\mu\text{m}$  technology ( $E_{CP} = 4E_{CN}$ ).

---

### Task 6.6

---

Calculate drain currents and threshold voltages of the CMOS Inverter.

- How large must the ratio  $W_P/W_N$  be for the inverter in Fig. 6.2 to have symmetrical pull-up and pull-down behavior ( $I_{DN}(\text{sat}) = I_{DP}(\text{sat})$ ).
- In standby mode, the NMOS should draw 50% less power. In this mode,  $V_{in} = V_{DD}$  and  $V_{out} = 0.5V$ . Which voltage must be  $V_{SB}$ ?

Use the values of a  $0.13\mu\text{m}$  technology.

---

### Task 6.7

---

Design a pseudo-NMOS inverter as shown in Fig. 6.3b with  $V_{OH} = V_{DD} = 1.8V$  and  $V_{OL} = 0.065V$ . Compare the voltage transfer characteristic (VTC) from a SPICE calculation with the results of a manual calculation. Use the values of a  $0.18\mu\text{m}$  technology.


---

### Task 6.8

---

Given are the CMOS and the pseudo-NMOS inverter in Fig. 6.3. Size the two inverters according to the following specification assuming that the load is  $50\text{fF}$ : CMOS Inverter -  $t_{PHL} = t_{PLH} < 50\text{ps}$ ,  $V_{OH} = 1.2V$ ,  $V_{OL} = 0V$ , low power consumption and minimum area; pseudo-NMOS Inverter -  $t_{PHL} < 50\text{ps}$ ,  $V_{OH} = 1.2V$ ,  $V_{OL} = 0.1V$ , low power consumption

---

 


**Figure 6.3:** Schematic CMOS Inverter (a) and Pseudo-NMOS Inverter (b)

and minimum area.  $V_{PHL} = 0.2V$ , pseudo-NMOS Inverter -  $t_{PHL} < 50ps$ ,  $V_{OH} = 1.1V$ ,  $V_{OL} = 0.1V$ , low power consumption and minimum area.

### Task 6.9

The two CMOS circuits in Fig. 6.4 are considered as tristate buffers. Discuss how these two circuits work as tristate buffers and which one is more suitable as a tristate buffer.

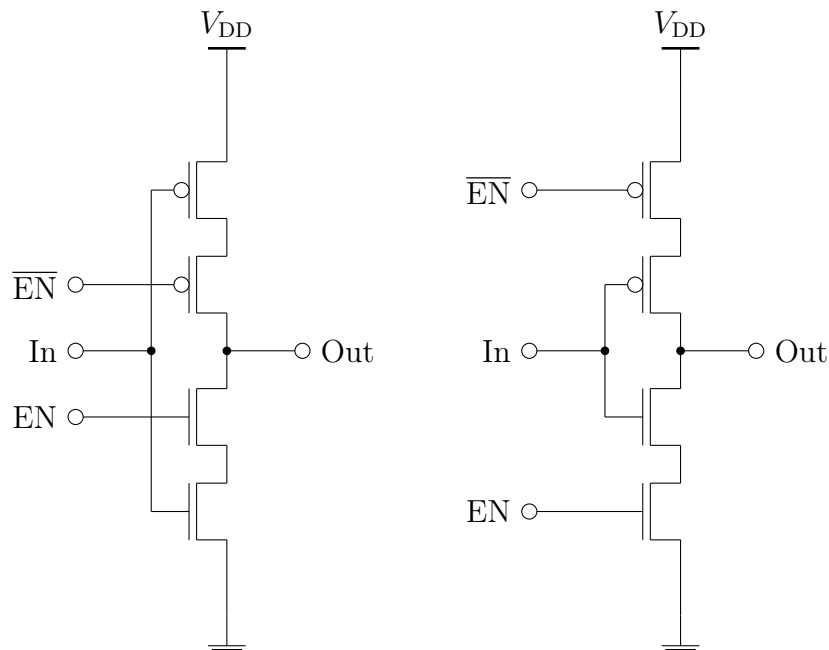

**Figure 6.4:** Tri-State Inverter