

Task 9.1

A CMOS inverter exhibits a pull-up transistor with $8\lambda:2\lambda$ (W/L) and a pull-down transistor with $4\lambda:2\lambda$ (W/L) in $0.18\mu\text{m}$ technology.

$$\begin{aligned} (\mu_n &= 270\text{cm}^2/\text{Vs}, & \mu_p &= 70\text{cm}^2/\text{Vs}, & C_{\text{ox}} &= 1.6\mu\text{F}/\text{cm}^2, & V_{\text{TN}} &= 0.5\text{V}, \\ V_{\text{TP}} &= -0.5\text{V}, & V_{\text{DD}} &= 1.8\text{V}, & L &= 200\text{nm}, & E_{\text{CN}}L_{\text{N}} &= 1.2\text{V}, \\ E_{\text{CP}}L_{\text{P}} &= 4.8\text{V}, & v_{\text{sat}} &= 8 \cdot 10^6\text{cm/s}) \end{aligned}$$

- Calculate the delay time (FO4) of an inverter for a step at the input. Line capacitances should be neglected.
- Calculate the delay time (FO1) of four inverters in chain for a step at the input. Consider different rise and fall times.

Task 9.2

Calculate τ_{inv} und γ_{inv} for an inverter in $0.13\mu\text{m}$ technology.

Task 9.3

Calculate the optimal fanout f for a three-level inverter chain ($C_{\text{load}} = 200\text{fF}$ and $C_{\text{in}} = 1\text{fF}$). Also calculate the value of f for the optimal number of levels. In both cases, calculate the delay through the inverter chain assuming $\tau_{\text{inv}}=7.5\text{ps}$ and $\gamma_{\text{inv}}=0.5$.

Task 9.4

Size the gates along the path indicated by the arrow in the circuitry in Fig. 9.1.

 


Figure 9.1: Optimum Delay along a Path

Task 9.5

Now size the gates from task 9.4 using Tab. 9.1 and Tab. 9.2 with Logical Effort (LE). Calculate the optimum delay first.

Type of Gate	1 input	2 input	3 input	4 input
INV	1	-	-	-
NAND	-	4/3	5/3	6/3
NOR	-	5/3	7/3	9/3

Table 9.1: Logical Effort (LE) of Simple Gates

Type of Gate	1 input	2 input	3 input	4 input
INV	$P_{\text{inv}} = 1/2$	-	-	-
NAND	-	$2P_{\text{inv}} = 1$	$3P_{\text{inv}} = 3/2$	$4P_{\text{inv}} = 2$
NOR	-	$3P_{\text{inv}} = 3/2$	$4.5P_{\text{inv}} = 9/4$	$6P_{\text{inv}} = 3$

Table 9.2: Parasitics (P) of Simple Gates

Task 9.6

For the specified circuitry in Fig. 9.2, determine the optimal stage effort and total path delay, and size the gates.

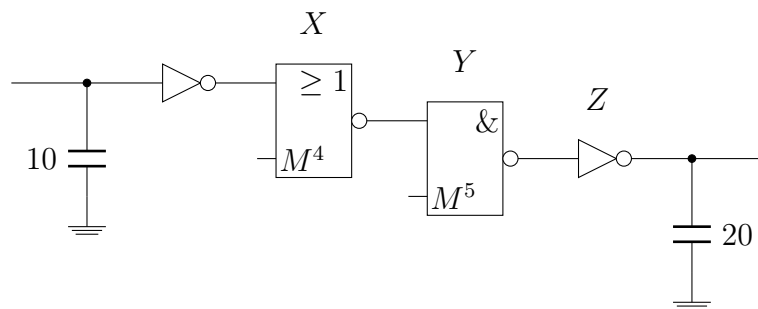


Figure 9.2: Optimal Stage Effort and Path Delay

Task 9.7

For each circuit in Fig. 9.3, determine the inherent capacitance C_{self} for an input step ($0.13\mu\text{m}$ technology).

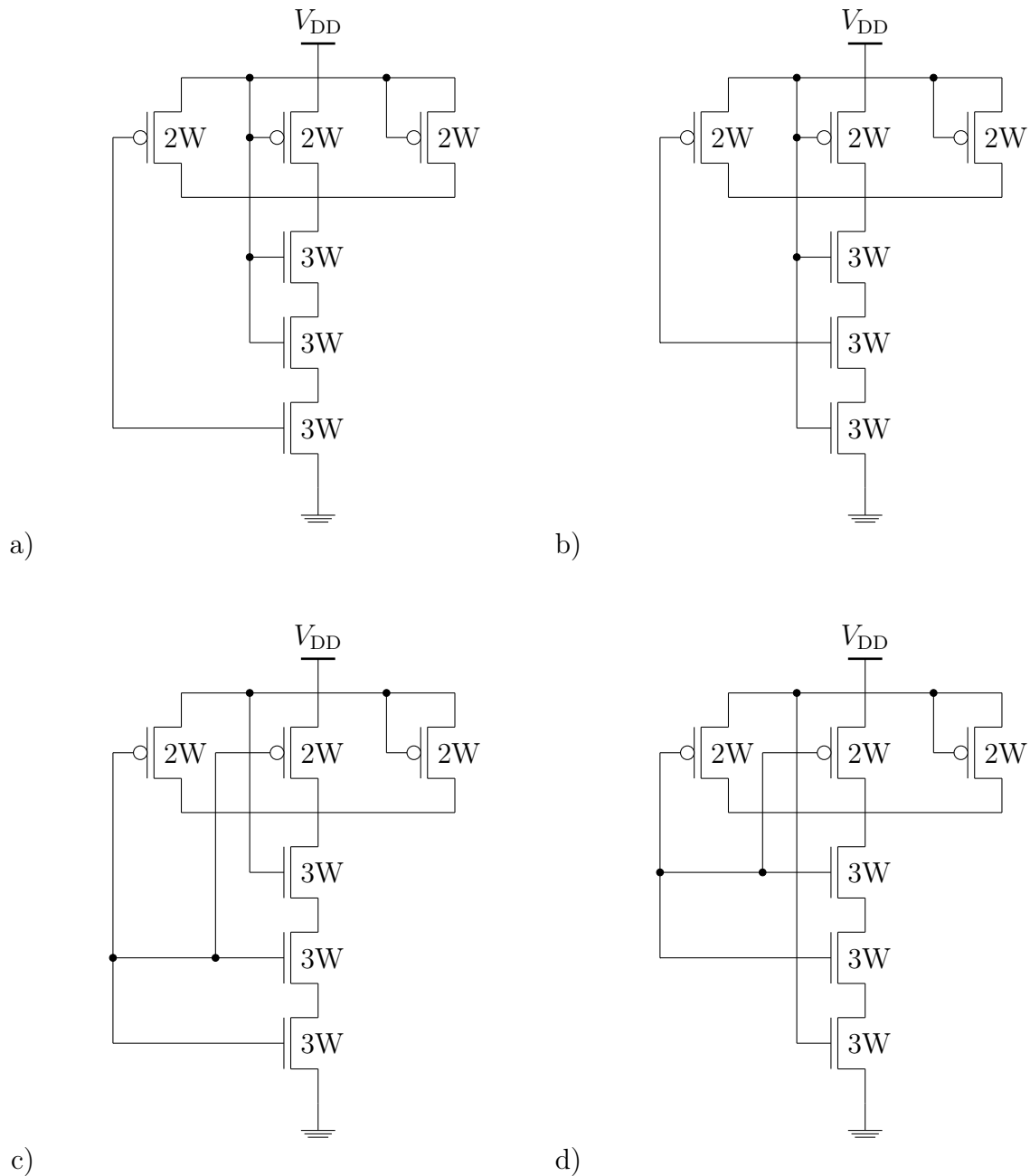


Figure 9.3: Calculation of the Internal Capacitance C_{self}