

Task 8.1

Calculate the power consumption of a pseudo NMOS inverter in its logical zero. Given $V_{OL} = 0.1V$ and $W_N/L_n = 9$ in $0.13\mu m$ technology ($\mu_n = 270\text{cm}^2/Vs$, $C_{ox} = 1.6\mu F/\text{cm}^2$, $V_{TN} = 0.4V$, $V_{DD} = 1.2V$, $L = 100\text{nm}$, $E_{CN}L_N = 0.6V$, $v_{sat} = 8 \cdot 10^6\text{cm/s}$).

Task 8.2

Calculate the power consumed on a chip:

- i) The chip has 10M gates, an activity factor of 10%, $V_{DD} = 1.8V$, a clock frequency of 500MHz and an average capacity per node of 20fF.
- ii) The chip has 50M gates, an activity factor of 5%, $V_{DD} = 1.2V$, a clock frequency of 1GHz and an average capacity per node of 10fF.

Explain which design is the better one and why?

 
Task 8.3

Figure 8.1: RC Circuit

Determine the total energy for the RC circuit in Fig. 8.1. This is transferred from the voltage source to the circuit when there is a jump from 0 to V_{DD} . Calculate the energy stored by the capacitor. What happens to the rest?

Task 8.4

Calculate R_{eqn} and R_{eqp} in $0.13\mu m$ technology ($\mu_n = 270\text{cm}^2/Vs$, $\mu_p = 70\text{cm}^2/Vs$, $C_{ox} = 1.6\mu F/\text{cm}^2$, $V_{TN} = 0.4V$, $V_{TP} = -0.4V$, $V_{DD} = 1.2V$, $L = 100\text{nm}$, $E_{CN}L_N = 0.6V$, $E_{CP}L_P = 2.4V$, $v_{sat} = 8 \cdot 10^6\text{cm/s}$).

Task 8.5

Determine the worst case capacities for the NAND3 in Fig. 8.2. Consider common areas for source and drain and specify the result depending on C_g and C_{eff} .

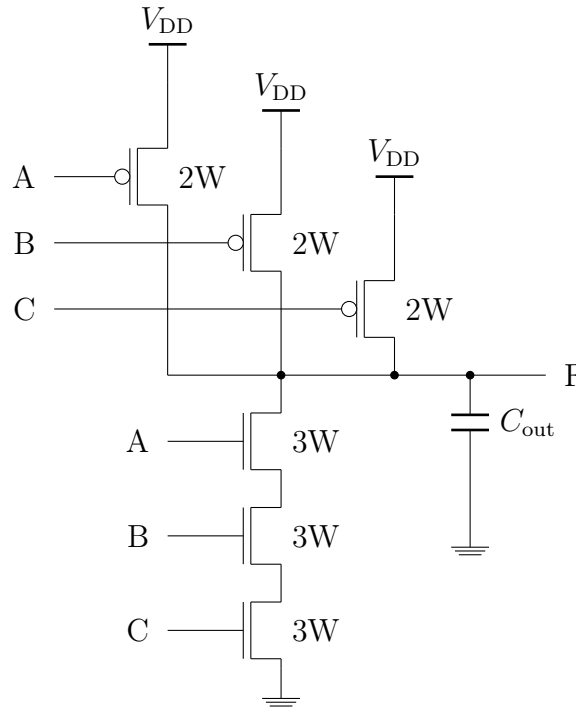


Figure 8.2: NAND3 Gate

Task 8.6

A CMOS inverter has a pull-up transistor with $8\lambda:2\lambda$ and a pull-down transistor with $4\lambda:2\lambda$. The inverter should be able to drive four identical inverters. Calculate all capacitances in $0.18\mu\text{m}$ technology ($\mu_n = 270\text{cm}^2/\text{Vs}$, $\mu_p = 70\text{cm}^2/\text{Vs}$, $C_{\text{ox}} = 1\mu\text{F}/\text{cm}^2$, $V_{\text{TN}} = 0.5\text{V}$, $V_{\text{TP}} = -0.5\text{V}$, $V_{\text{DD}} = 1.8\text{V}$, $L = 200\text{nm}$, $E_{\text{CN}}L_{\text{N}} = 1.2\text{V}$, $E_{\text{CP}}L_{\text{P}} = 4.8\text{V}$, $v_{\text{sat}} = 8 \cdot 10^6\text{cm/s}$), line capacitances are neglected.

Task 8.7

Specify the structure (schematic of building blocks (gates)) of a positive edge controlled RS-FF. Set up the switching sequence table. In addition, enter a positive edge-controlled D-FF. How can the input capacitance be reduced?