

Task 12.1

Determine the function of the gate in figure 12.1. Which clock feedthrough is generated for the parameters of a $0.13\mu\text{m}$ technology at internal node X and which worst-case voltage due to charge sharing. Is there a potential risk?

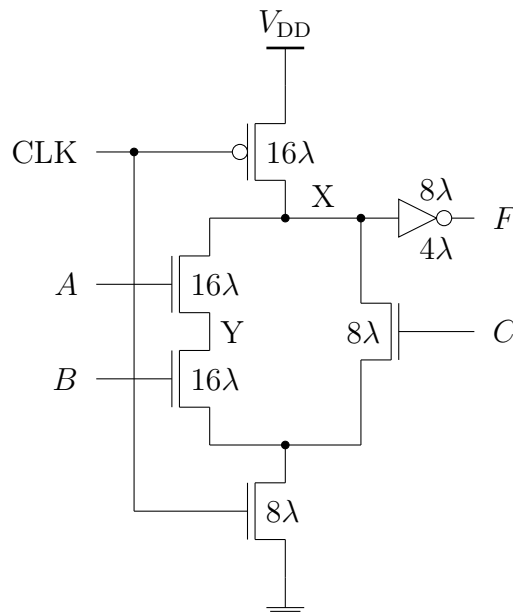


Figure 12.1: Gates in Domino Logic

Task 12.2

Design the minimal XOR/XNOR function in Dual-Rail Domino Logic

Task 12.3

Design minimal logic circuits from transfer gates for the following functions:

a) $F = A \vee BC$

b) $F = AB \vee BC \vee \bar{C}$

c) $F = (\overline{A \vee B \vee C}) \vee \overline{A}B$

c) $F = (\overline{A \vee B \vee C}) \vee \overline{A}B$

d) $F = \left(\overline{(\overline{A \vee B \vee C}) \vee \overline{A}B} \right)$

Task 12.4

Describe the function of each circuit in Fig. 12.2 by its truth table.

 


Figure 12.2: Circuits using Transfer Gates

Task 12.5

Design in Domino Logic:

a) $F = \bar{A} \vee \bar{B}C$

b) $F = A\bar{B} \vee BC \vee \bar{C}$

c) $F = (\overline{\bar{A} \vee \bar{B} \vee C}) \vee A\bar{B}$

d) $F = \left(\overline{(\bar{A} \vee \bar{B} \vee C)} \vee A\bar{B} \right)$