 



**Task 10.1**

Explain the difference between clock feedthrough and charge sharing.

**Task 10.2**

**Figure 10.1:** Multi-Voltage-Array

Calculate the Voltage at all nodes of the Multi-Voltage-Array in Figure 10.1 taking into account the body effect. All nodes are at 0V at the beginning. Use the values of a  $0.13\mu\text{m}$  technology ( $2|\Phi_F| = 0.88\text{V}$ ,  $\gamma = 0.2\text{V}^{1/2}$ ,  $V_T = 0.4\text{V}$ ,  $V_{DD} = 1.2\text{V}$ ).

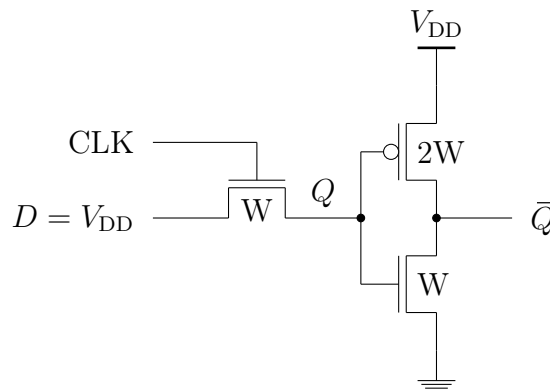**Task 10.3**

**Figure 10.2:** Dynamic (Positive Edge Controlled) D-Latch


For the dynamic D latch in Fig. 10.2, estimate the output voltages for  $Q$  and  $\bar{Q}$ , for the clock (CLK) at the input from LOW (GND) to HIGH ( $V_{DD}$ ) and HIGH ( $V_{DD}$ ) to LOW (GND). Consider Clock Feedthrough. Use the parameters of a  $0.18\mu\text{m}$  CMOS technology. ( $W = 200\text{nm}$ ,  $\mu_n = 270\text{cm}^2/\text{Vs}$ ,  $\mu_p = 70\text{cm}^2/\text{Vs}$ ,  $C_{ox} = 1\mu\text{F}/\text{cm}^2$ ,  $V_{TN} = 0.5\text{V}$ ,  $V_{TP} = -0.5\text{V}$ ,  $V_{DD} = 1.8\text{V}$ ,  $L = 200\text{nm}$ ,  $E_{CN}L = 1.2\text{V}$ ,  $E_{CP}L = 4.8\text{V}$ ,  $v_{sat} = 8 \cdot 10^6\text{cm/s}$ )

---

**Task 10.4**

---

Add Source (S), Drain (D) and the value of  $V_{\text{out}}$  to the pass transistors.

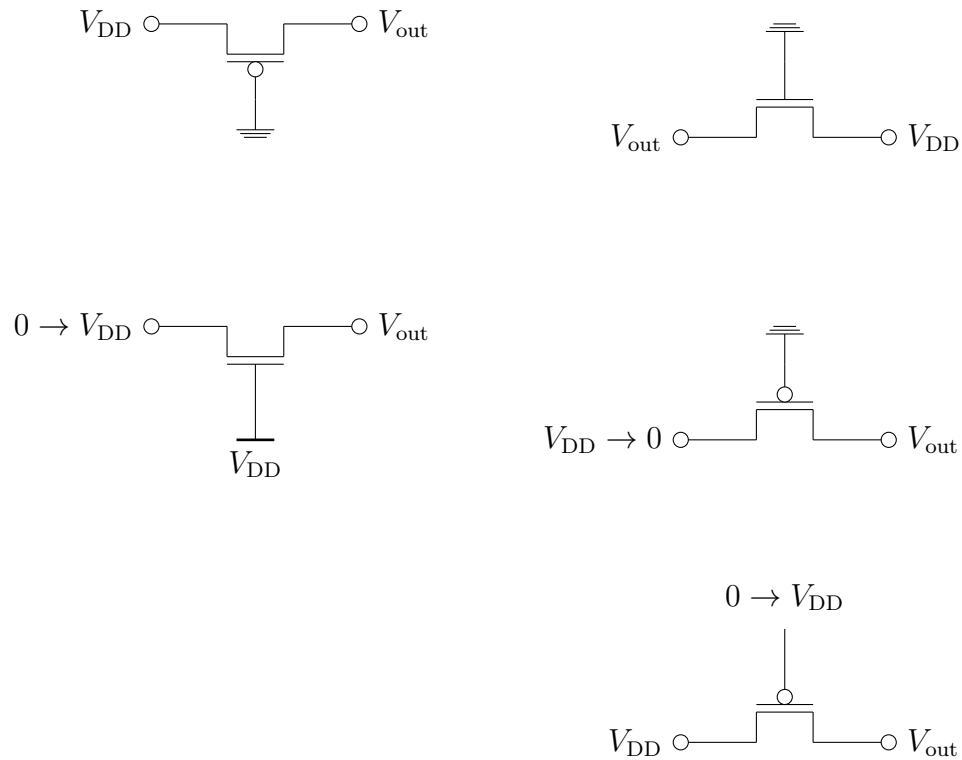

**Figure 10.3:** Operating States of Pass Transistors